

Vincent Han

Midterm 2

Problem 1:

```
module expl_beh(x, y, a, b, c);
    input a, b, c;
    output x, y;

    wire na, nb, nc;
    not #(1) n1(na, a);
    not #(1) n2(nb, b);
    not #(1) n3(nc, c);


    wire t3, t5, t6;
    and #(1) a1(t3, na, b, c);
    and #(1) a2(t5, a, nb, c);
    and #(1) a3(t6, a, b, nc);

    reg x_out, y_out;
    always @(t3, t6)
        x_out = t3 | t6;
    always @(a, t5)
        y_out = a | #(3) t5;


    assign x = x_out;
    assign y = y_out;
endmodule
```

Problem 2:


Code A:

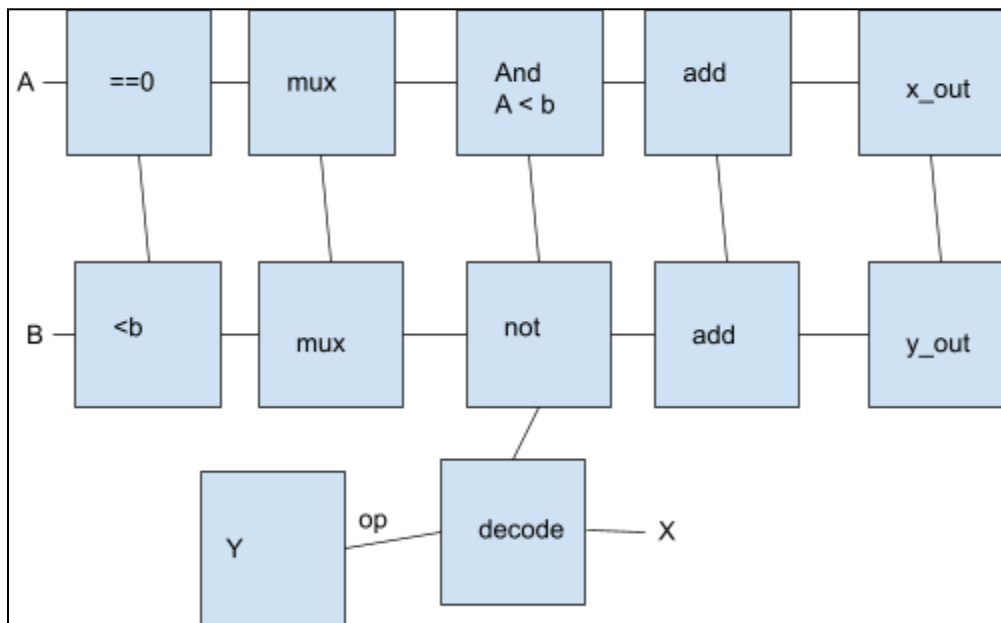

Code B:

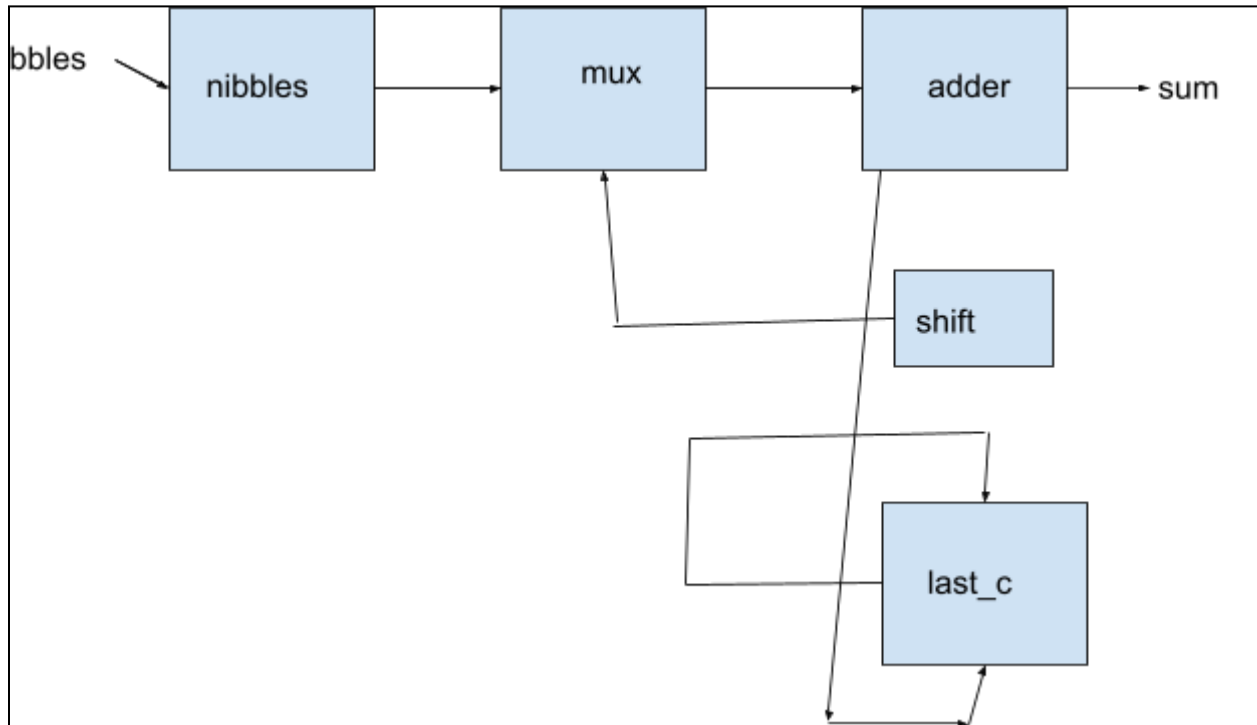

 Problem 3: Show how to implement with 2 LUT4s and a 2-1 MUX.



1. LUT1: This LUT takes inputs b, c, d, and e. It is programmed to implement the function $f_1(b, c, d, e)$ based on the truth table of $f(a, b, c, d, e)$ where $a = 0$ (complemented value). The output of LUT1 represents $f_1(b, c, d, e)$.
2. LUT2: This LUT also takes inputs b, c, d, and e. It is programmed to implement the function $f_2(b, c, d, e)$ based on the truth table of $f(a, b, c, d, e)$ where $a = 1$. The output of LUT2 represents $f_2(b, c, d, e)$.
3. MUX: The 2-1 MUX takes the outputs of LUT1 and LUT2 as its inputs. The selection input of the MUX is a. When $a = 0$, the output of LUT1 ($f_1(b, c, d, e)$) is selected as the output of the MUX. When $a = 1$, the output of LUT2 ($f_2(b, c, d, e)$) is selected as the output of the MUX.

LUT1 ($f_1(b, c, d, e)$):
 Inputs: b, c, d, e
 Output: $f_1(b, c, d, e)$

LUT2 ($f_2(b, c, d, e)$):
 Inputs: b, c, d, e
 Output: $f_2(b, c, d, e)$

MUX:
 Inputs: $f_1(b, c, d, e)$, $f_2(b, c, d, e)$, a
 Output: $f(a, b, c, d, e)$

Problem 4:

(a) Initial Contents:
 Product Register (12 bits): 00000000 101010 (Initial multiplier "10 1001" loaded in the least significant 6 bits)
 Multiplicand Register (6 bits): 000010 (Multiplicand "10 1010")

(b) Arithmetic and Shift Operations for each iteration:

1. Initial Step:
 - Product Register: 00000000 101010 (Multiplier)
 - Multiplicand Register: 000010 (Multiplicand)
2. Iteration 1:
 - Right Shift (Shift multiplier one position to the right)
 - Product Register: 00000001 010100 (After Shift)
 - Add (Since the last bit of the multiplier is 1, add the multiplicand to the product register)
 - Product Register: 00001011 101100 (After Add)

```
3. Iteration 2:
  - Right Shift
  - Product Register: 00000101 110110 (After Shift)
  - Add
  - Product Register: 00010111 011000 (After Add)

4. Iteration 3:
  - Right Shift
  - Product Register: 00001011 101100 (After Shift)
  - Add
  - Product Register: 00110011 110000 (After Add)

5. Iteration 4:
  - Right Shift
  - Product Register: 00011001 111000 (After Shift)
  - No Add (Since the last bit of the multiplier is 0, no addition is performed)

6. Iteration 5:
  - Right Shift
  - Product Register: 00001100 111100 (After Shift)
  - No Add

7. Iteration 6:
  - Right Shift
  - Product Register: 00000110 011110 (After Shift)
  - Add
  - Product Register: 00111001 011100 (After Add)
```

```
(c) Contents of the Product Register after the first iteration:
Product Register: 00001011 101100 (After the first iteration)
```

Problem 5:

```

module multiplier(
    input wire signed [7:0] M, // Multiplicand
    input wire signed [7:0] Q, // Multiplier
    output reg signed [7:0] A, // Accumulator
    input wire [3:0] n, // Counter
    output reg done // Done
);

    localparam [2:0]
        S_START = 3'b000,
        S_INIT = 3'b001,
        S_CHECK_Q = 3'b010,
        S_SUBTRACT = 3'b011,
        S_ADD = 3'b100,
        S_SHIFT = 3'b101,
        S_CHECK_N = 3'b110,
        S_STOP = 3'b111;

    reg [2:0] state, next_state;
    always @(posedge clk) begin
        if (reset)
            state <= S_START;
        else
            state <= next_state;
        end

        // Output register to hold the result (Qres)
        reg signed [7:0] Qres;

        input wire clk, reset;

```

```

always @* begin
    case (state)
        S_START: next_state = S_INIT;
        S_INIT: next_state = S_CHECK_Q;
        S_CHECK_Q: next_state = (Q[1:0] == 2'b10) ? S_SUBTRACT : S_ADD;
        S_SUBTRACT: next_state = S_SHIFT;
        S_ADD: next_state = S_SHIFT;
        S_SHIFT: next_state = S_CHECK_N;
        S_CHECK_N: next_state = (n == 4'b0000) ? S_STOP : S_CHECK_Q;
        S_STOP: next_state = S_STOP;
        default: next_state = S_START;
    endcase
end

```

```

always @(posedge clk) begin
    case (state)
        S_START: begin
            A <= 0;
            Qres <= 0;
            done <= 0;
        end
        S_INIT: begin
            A <= 0;
            Qres <= 0;
            done <= 0;
        end
        S_CHECK_Q: begin
        end
        S_SUBTRACT: begin
            A <= A - M;
        end
        S_ADD: begin
            A <= A + M;
        end
        S_SHIFT: begin
            {Q, Qres, A} <= {Q[0], A[7:1], Q[7]};
            n <= n - 1;
        end
        S_CHECK_N: begin
        end
        S_STOP: begin
            done <= 1;
        end
        default: begin
        end
    endcase
end

```