 


Vincent Han

Homework 1

EE 4301

2.4 Write a Verilog description of the following combinational circuit using concurrent statements. Each gate has a 5-ns delay, excluding the inverter, which has a 2-ns delay.



```
module question1(A,B,C,D,Z)
    input A, B, C, D;
    output Z;
    wire E, F, G, H, I;
    assign #5 G = A & B & C;
    assign #5 H = ~(B | C);
    assign #5 E = D | G;
    assign #5 F = ~(A & H);
    assign #2 I = ~F;
    assign #5 Z = I ^ E;
end module
```

2.8 (a) What device does the following Verilog code represent?

```
always @(CLK, Clr, Set)
begin
    if(Clr == 1'b1)
        Q <= 1'b0;
    else if(Set == 1'b1)
        Q <= 1'b1;
    else if(CLK == 1'b0)
        Q <= D;
    else begin
        end
end
```

(b) What happens if $Clr = Set = 1$ in the device in part a?

- a. Falling edge flip-flop that has async active high clear and set
- b. Since Q has less priority than Clr, Q will be 0

- 2.14** In the following Verilog process *A*, *B*, *C*, and *D* are all registers that have a value of 0 at time = 10ns. If *E* changes from 0 to 1 at time = 20ns, specify the time(s) at which each signal will change and the value to which it will change. List these changes in chronological order.

```

always @(E)
begin
    A <= #5 1;
    B <= A + 1;
    C <= #10 B;

    D <= #3 B;
    A <= #15 A + 5;
    B <= B + 7;
end

```


| Time | 10ns | 20ns | 20ns + D | 23ns | 25ns | 35ns |
|----------|------|------|----------|------|------|------|
| Variable | | | | | | |
| A | 0 | 0 | 0 | 0 | 1 | 5 |
| B | 0 | 0 | 7 | 7 | 7 | 7 |
| C | 0 | 0 | 0 | 0 | 0 | 0 |
| D | 0 | 0 | 0 | 0 | 0 | 0 |
| E | 0 | 1 | 1 | 1 | 1 | 1 |

- 2.21** Draw the hardware obtained if the following code is synthesized:

```

module reg3 (Q1,Q2,Q3,Q4, A,CLK);
input A;
input CLK;
output Q1,Q2,Q3,Q4;
reg Q1,Q2,Q3,Q4;
always @(posedge CLK)
begin
    Q4 = Q3;
    Q3 = Q2;
    Q2 = Q1;
    Q1 = A;
end
endmodule

```

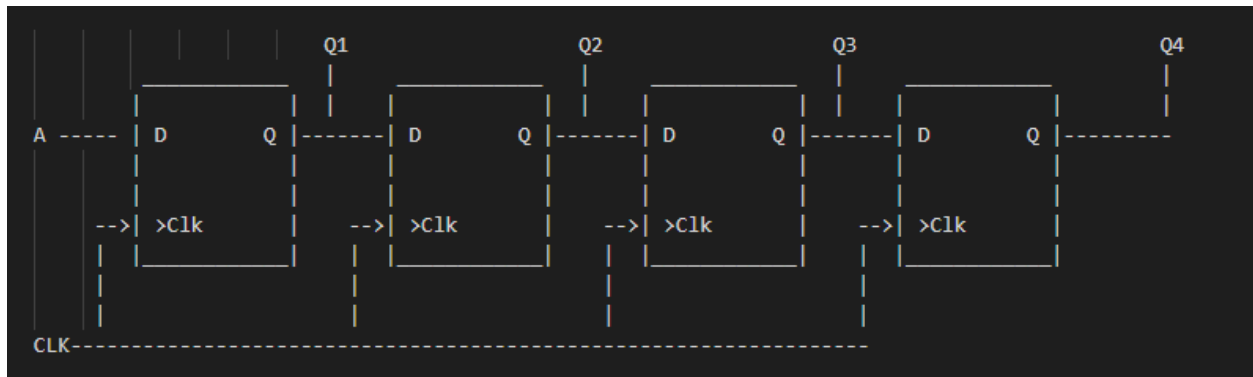

- 2.24 (a) Assume $D_1=0$, $D_2=5$, and D_1 changes to 1 at time=10ns. What are the values of D_1 and D_2 after the following code has been executed once? Do the values of D_1 and D_2 swap?

```
always @ (D1)
begin
    D2 <= D1;
    D1 <= D2;
```

End

- (b) Assume $D_1=0$, $D_2=5$, and D_1 changes to 1 at time=10ns. What are the values of D_1 and D_2 after the following code has been executed once? Do the values of D_1 and D_2 swap?

```
always @ (D1)
begin
    D2 = D1;
    D1 = D2;
end
```

- (c) How many latches will result when the following code is synthesized? Assume B is 3 bits long.

```
always @ (State) begin
    case(State)
        2'b00: B = 5;
        2'b01: B = 3;
        2'b10: B = 0;
    endcase
end
```

Circle the correct choice:

- i. 1 latch because 1 case is missing
- ii. 2 latches because state is 2 bits
- iii. 3 latches because B is 3 bits
- iv. 5 latches because B is 3 bits and state is 2 bits
- v. None of the above. But it results in _____ latches.

a. Yes they do swap, D1 = 5 and D2 = 1

b. No they do not swap, D1 = 1 = D2

c. Option iii

2.34 Consider the following Verilog code:

```
module Q3(A,B,C,F,Clk,E);  
  input A,B,C,F,Clk;  
  output reg E;  
  
  reg D,G;  
  
  initial  
  begin  
    E = 1'b0;  
    D = 1'b0;  
    G = 1'b0;  
  end  
  
  always @(posedge Clk)  
  begin  
    D <= A & B & C;  
    G <= ~A & ~B;  
    E <= D | G | F;  
  end  
endmodule
```

- (a) Draw a block diagram for the circuit (no gates and at block level only).
- (b) Give the circuit generated by the preceding code (at the gate level).

